

VE270 RC Week 5

Combinational Circuit

Shi Li

2019.10.9

Combinational Circuit

- The output depends only upon the present combination of its inputs
- Input change \Leftrightarrow Output change

Combinational Circuit compared with Sequential Circuit

- Truth table for a combinational circuit

p	q	$p \vee q$
T	T	T
T	F	T
F	T	T
F	F	F

- Characteristic table for a sequential circuit

S(t)	R(t)	Q(t)	Q(t+ Δ)	\longrightarrow Q ⁺
0	0	0	0	hold
0	0	1	1	
0	1	0	0	reset
0	1	1	0	
1	0	0	1	set
1	0	1	1	
1	1	0	X	not allowed
1	1	1	X	

Design Process

- Capture the function
 - truth table/equation from requirements
- Convert to equation
 - k-map logic optimization
- Implement the circuit
 - from the optimized logic expression

Design Process

Exercise 1 (modified from 2018 Fall RC Slides)

- Now imagine that you are the smart tech support for a spy, you have to design a lock for his secret suitcase:
 - Each input is a 4-bit binary number $x_1x_2x_3x_4$;
 - 1010 opens the suitcase;
 - 0100, 0101, 1100, 1101, 1111 blows the suitcase up (doesn't matter whether the suitcase opens or not);
 - Output x for whether to open the suitcase and y for whether to make it explode

Design Process

Exercise 1 (modified from 2018 Fall RC Slides)


- Step 1. Capture the function
 - $x = x_1x_2'x_3x_4'$
 - $y = x_1'x_2x_3'x_4' + x_1'x_2x_3'x_4 + x_1x_2x_3'x_4' + x_1x_2x_3'x_4 + x_1x_2x_3x_4$
- Step 2. Convert the equation
 - We use k-map to simplify the expression for y.
 - $y = x_2x_3' + x_1x_2x_4$

		x1x2			
		00	01	11	10
x3x4	00	0	1	1	0
	01	0	1	1	0
	11	0	0	1	0
	10	0	0	0	0


Design Process

Exercise 1 (modified from 2018 Fall RC Slides)

- Step 3. Implement the circuit

 


- We can further simplify it.

 

Combinational Building Blocks

1. MUX

 - Example: 4 to 1 Mux
- Using 2 “switches” to choose one of the four input signals





- Question: If we have 35 input from i_0 to i_{34} , how much “switches” do we need?
- Answer: 6 ($i_{35} \sim i_{63}$ can be seen as don't cares)

Combinational Building Blocks

2. Adder: Half Adder




A	B	Sum	Carry
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

  

Combinational Building Blocks

 
2. Adder: Full Adder

- The first way to implement a full adder.



A	B	C	Sum	Carry
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

 
$$\begin{aligned}\text{Sum} &= A'B'C + A'BC' + AB'C' + ABC \\ &= \Sigma m(1, 2, 4, 7) \\ \text{Carry} &= A'BC + AB'C + ABC' + ABC \\ &= \Sigma m(3, 5, 6, 7)\end{aligned}$$



Combinational Building Blocks

2. Adder: Full Adder

- Is there any way to make it simpler?

 


Question: Why use OR gate here?

Answer: Because the two H.A. cannot generate 1 at the same time. An OR gate is enough to deal with all the cases.

Combinational Building Blocks

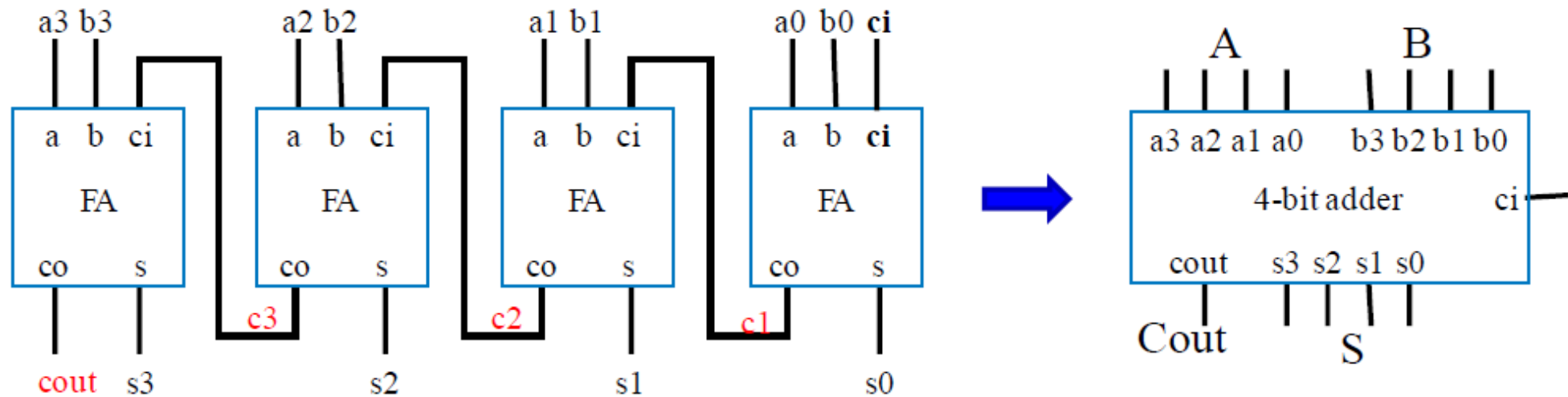2. Adder: Carry-Ripple Adder


- For a carry-ripple adder with 4-bit input, it generates 5-bit output.



Combinational Building Blocks

 2. Adder: Subtractor (for 2's complement numbers)

- When we do subtraction, we need to
- 1. add inverters to B input
- 2. set C0 to 1




Combinational Building Blocks

Exercise 2

- Use 2-1 muxes to design a simple 4-bit Arithmetic-Logic Unit.
- The input is ~~Cin~~, $A_0 \sim A_3$, $B_0 \sim B_3$, X . (My mistake, cin is not needed)
- The output is Cout, Overflow, $S_0 \sim S_3$.
- Specifications: When $X=1$, $S=A+B$. When $X=0$, $S=A-B$.
- You do not need to draw the complete circuit. Use blocks (mux, full adder, etc) instead.

Combinational Building Blocks

Exercise 2

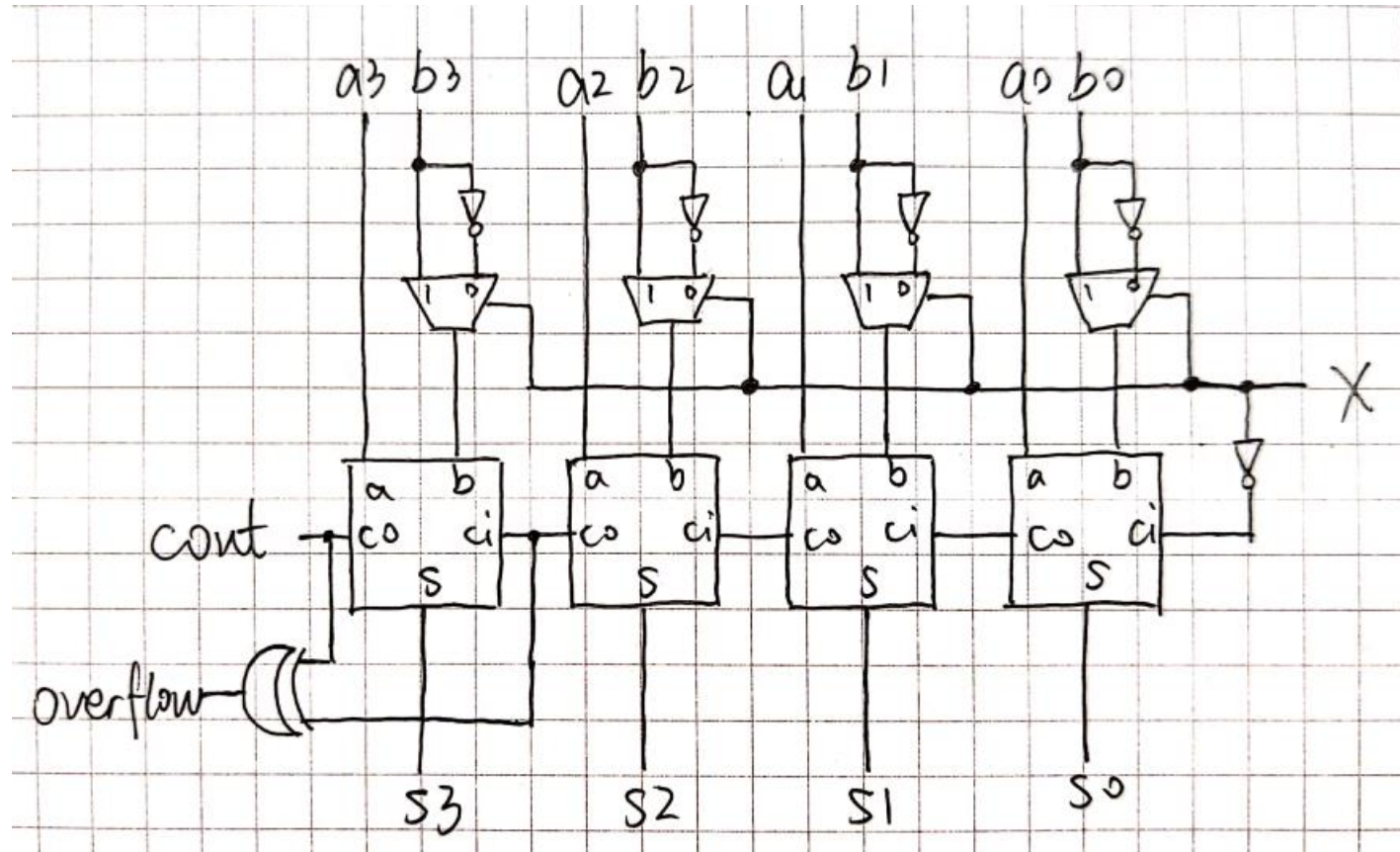

Combinational Building Blocks

3. Encoder & Decoder



Inputs								Outputs		
D ₀	D ₁	D ₂	D ₃	D ₄	D ₅	D ₆	D ₇	x	y	z
1	0	0	0	0	0	0	0	0	0	0
0	1	0	0	0	0	0	0	0	0	1
0	0	1	0	0	0	0	0	0	1	0
0	0	0	1	0	0	0	0	0	1	1
0	0	0	0	1	0	0	0	1	0	0
0	0	0	0	0	1	0	0	1	0	1
0	0	0	0	0	0	1	0	1	1	0
0	0	0	0	0	0	0	1	1	1	1

Inputs			Outputs							
x	y	z	D ₀	D ₁	D ₂	D ₃	D ₄	D ₅	D ₆	D ₇
0	0	0	1	0	0	0	0	0	0	0
0	0	1	0	1	0	0	0	0	0	0
0	1	0	0	0	1	0	0	0	0	0
0	1	1	0	0	0	1	0	0	0	0
1	0	0	0	0	0	0	1	0	0	0
1	0	1	0	0	0	0	0	1	0	0
1	1	0	0	0	0	0	0	0	1	0
1	1	1	0	0	0	0	0	0	0	1

Combinational Building Blocks

  3. Encoder & Decoder



- Decoder: N inputs, 2^N outputs
- Enable e (Question: How to implement it in the circuit?)
- Use decoder to implement any combinational circuit



Combinational Building Blocks

  3. Encoder & Decoder


- Decoder: N inputs, 2^N outputs
- Enable e (Question: How to implement it in the circuit? – Red lines)
- Use decoder to implement any combinational circuit




Combinational Building Blocks

 4. Buffer & Tri-state Buffer


- Why we use buffers?
 - Amplify the driving capability of a signal
 - Insert delay
 - Protect input from output
- Why we use tri-state buffer?
 - Provide another state “Z”
 - Z: high impedance



B	A	C
0	0	Z
0	1	Z
1	0	0
1	1	1

 

B	A	C
0	0	Z
0	1	Z
1	0	1
1	1	0

 

B	A	C
0	0	0
0	1	1
1	0	Z
1	1	Z