


VE270 FINAL RC

Arithmetic Components & Timing Issues

VE270 TA Group

Incrementer

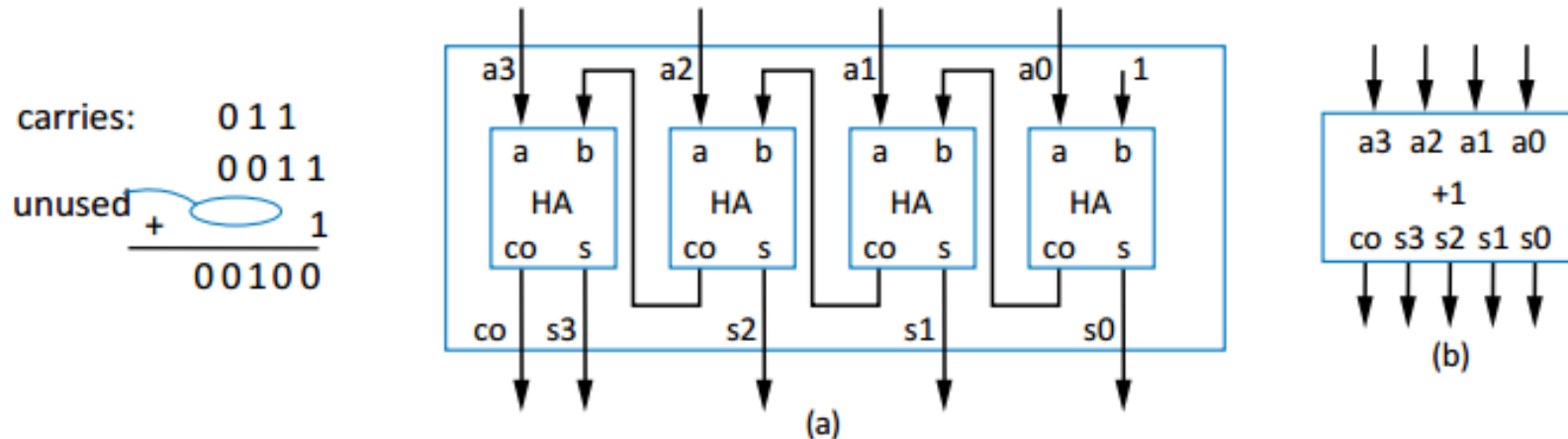- Traditional design: Capture truth table & derive equation → truth table grows exponentially for large operand
- Alternative design: use N-bit adder with one of the inputs set to 1 → slower but simpler





Inputs				Outputs				
a3	a2	a1	a0	c0	s3	s2	s1	s0
0	0	0	0	0	0	0	0	1
0	0	0	1	0	0	0	1	0
0	0	1	0	0	0	0	1	1
0	0	1	1	0	0	1	0	0
0	1	0	0	0	0	1	0	1
0	1	0	1	0	0	1	1	0
0	1	1	0	0	0	1	1	1
0	1	1	1	0	1	0	0	0
1	0	0	0	0	1	0	0	1
1	0	0	1	0	1	0	1	0
1	0	1	0	0	1	0	1	1
1	0	1	1	0	1	1	0	0
1	1	0	0	0	1	1	0	1

Comparator

- Outputs 1 if two N-bit numbers are equal
- Recall functionality of XNOR: outputs 1 if two operands are equal

0110 = 0111 ?

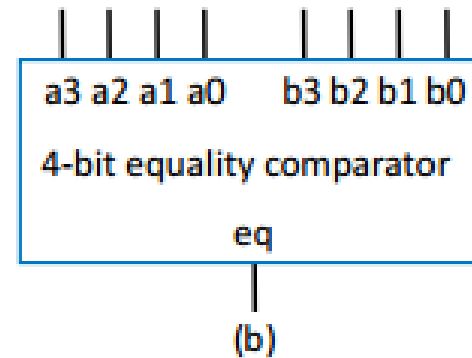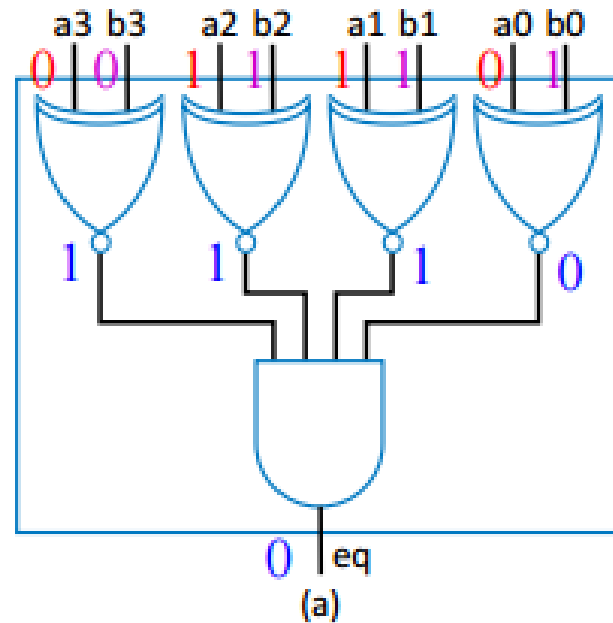

Magnitude Comparator

- Indicates whether $A > B$, $A = B$, or $A < B$, for its two N-bit inputs A and B
- Start at left, compare each bit pair, pass results to the right
- At each stage:
 - $\text{out_gt} = \text{in_gt} + (\text{in_eq} * a * b')$
 - $\text{out_lt} = \text{in_lt} + (\text{in_eq} * a' * b)$
 - $\text{out_eq} = \text{in_eq} * (a \text{ XNOR } b)$



A=1011 B=1001

1011 1001 Equal

1011 1001 Equal

1011 1001 Unequal


So $A > B$

 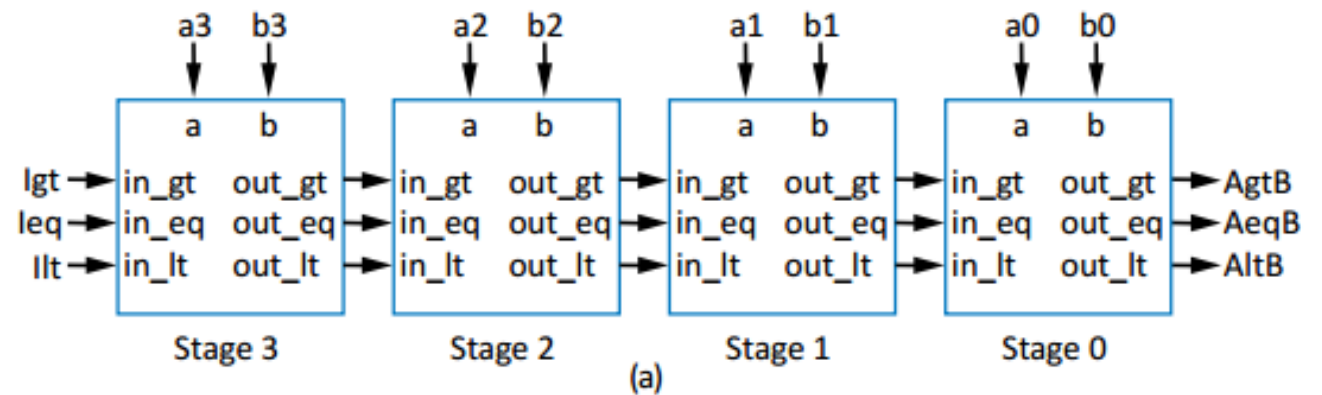

Multiplier

- Mimics multiplication by hand

0110					a3	a2	a1	a0	
0011					x b3	b2	b1	b0	
----	-----								
0110					b0a3	b0a2	b0a1	b0a0	(pp1)
0110				b1a3	b1a2	b1a1	b1a0	0	(pp2)
0000			b2a3	b2a2	b2a1	b2a0	0	0	(pp3)
+0000	+	b3a3	b3a2	b3a1	b3a0	0	0	0	(pp4)
-----	-----								
00010010	p7	p6	p5	p4	p3	p2	p1	p0	

 


Block symbol

need 3 adders

Smaller Multiplier -- Sequential (Add-and-Shift) Style

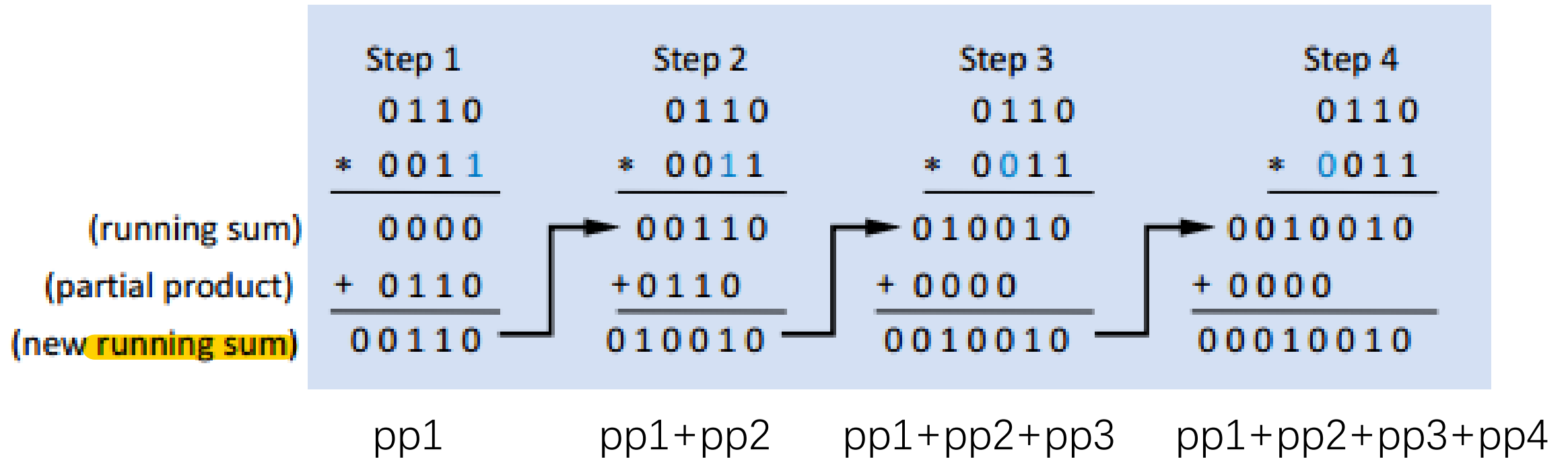- Compute one partial product at a time and maintain a running sum





only need 1 adder, but need more time

Timing issue

- Timing requirements for FSM
- Setup time and hold time
- Asynchronous input and metastability
- Synchronizer
- Switch debouncing
- Clock skew
- Hazards



Clocking Methodology for FSM

 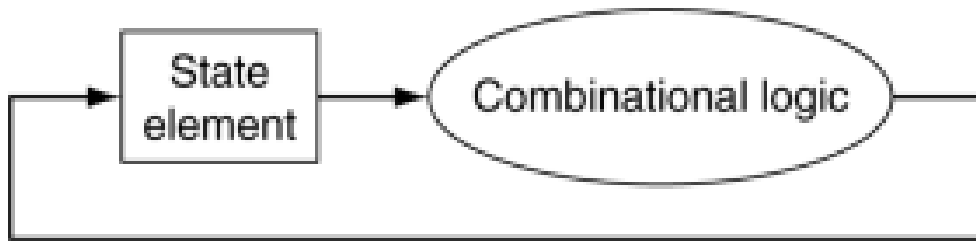- Clock cycles should be
 - Long enough to allow combinational logic completes computation
 - Longest delay determines clock period
 - Short enough to ensure acceptable performance and to capture small changes on external inputs





Setup time & hold time

  - Setup Time
 - Minimum time that data must be stable prior to the triggering edge
 - Fix: stretch clock, optimize combinational circuit
- Hold Time:
 - Minimum time that data must remain stable after the triggering edge
 - Fix: insert buffers




Metastable state & asynchronous inputs

 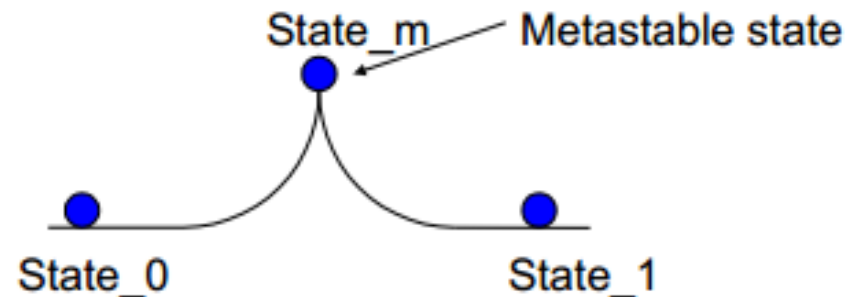- Synchronous system may be driven by asynchronous inputs which may put flip flops into the metastable state
- General rule: Ensure that all inputs are synchronous, i.e. synchronize them to the clock signal. Reset and set can be exceptions.




Synchronizer

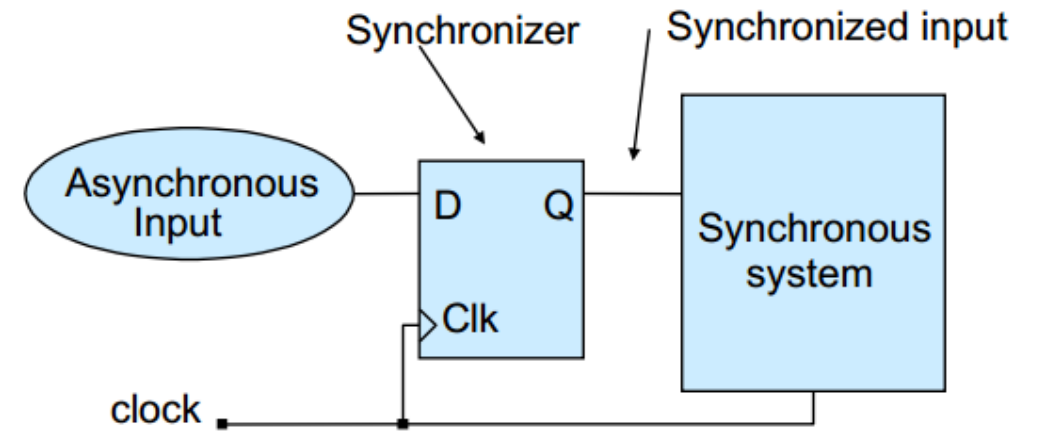- Use a D-type flip flop to synchronize the input.
- Synchronizer failure: The flip-flop may be in metastable state, then its state will be nondeterministic, its output may enter a metastable state and is not synchronized anymore



Reduce possibility of synchronizer failure

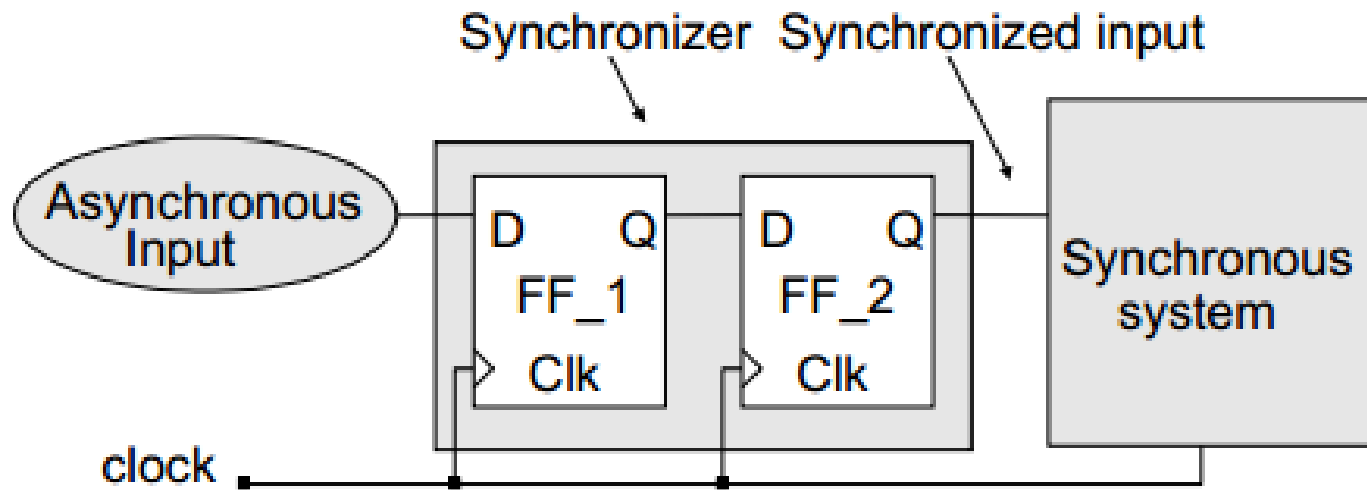- Stretch the clock period to allow more time for the circuit to recover → less synchronizer failure, but slower circuit
- Double DFF synchronizer: The first flip-flop might enter a metastable state, but has a clock period to recover. Both flip-flop must enter a metastable state to have a synchronizer failure.




Switch debouncing

- SR Latch
 - When throw is at position 0, $S = 1$, $R = 0$, Data = 0
 - When throw changes to position 1 $R = 1$, $S = (0 \leftrightarrow 1)$
Data = 1



S	R	Q	Q ⁺
0	0	0	X
0	0	1	X
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	1

not allowed
set
reset
hold

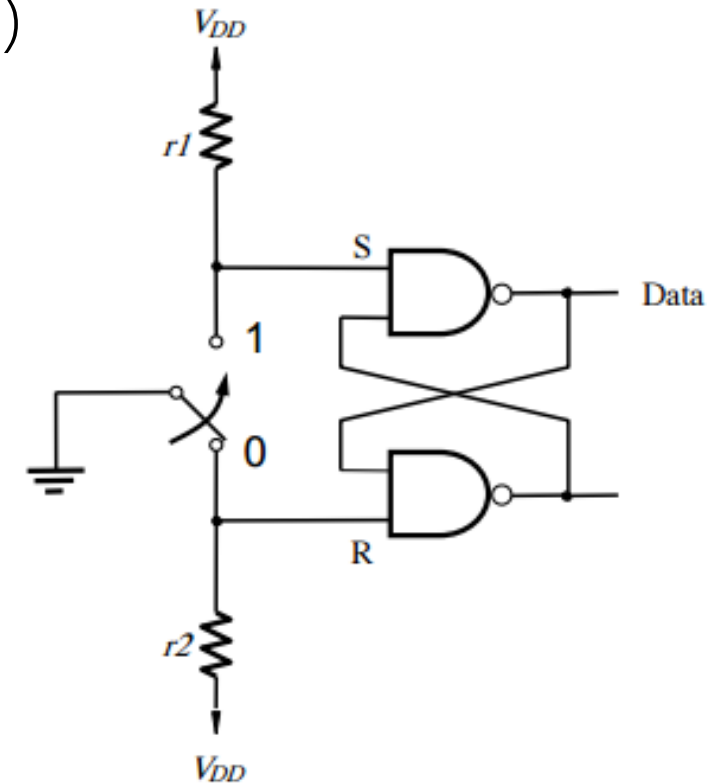

Switch debouncing

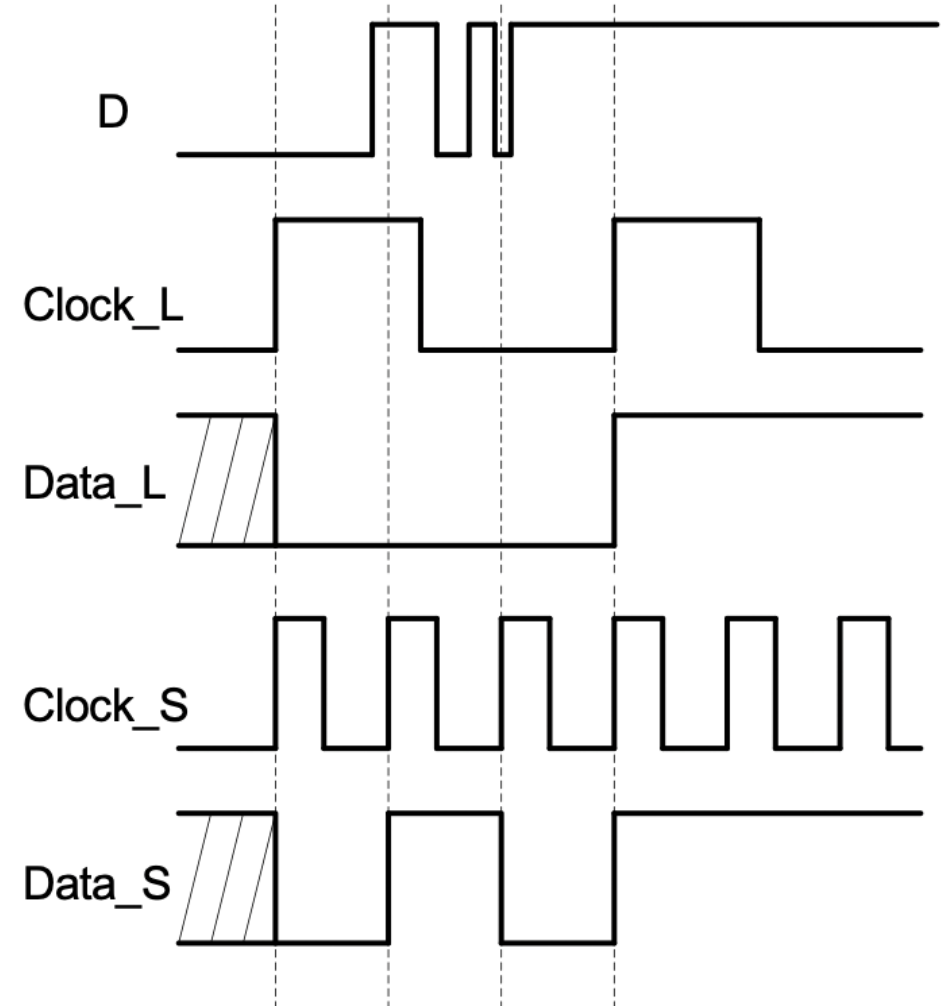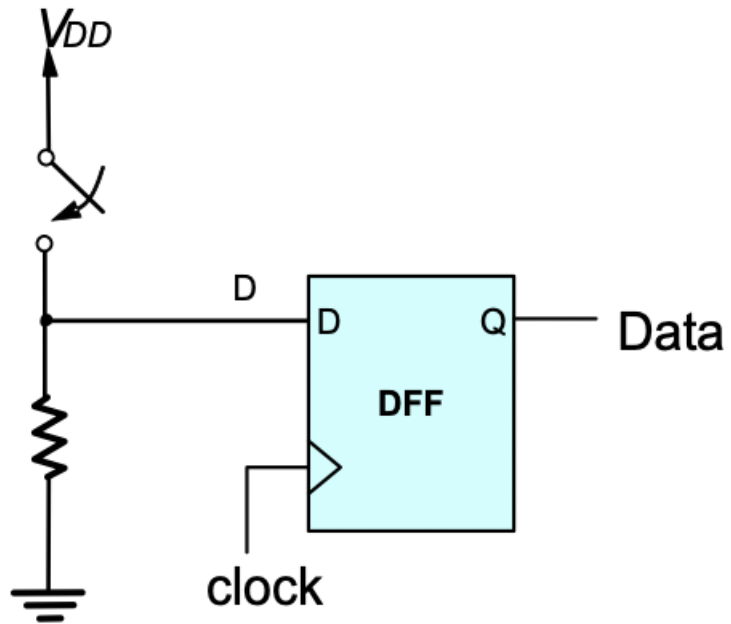- D Flip Flop: clock needs careful design




Clock skew

- The situation in which the clock signal arrives at different flip flops at different times is known as clock skew
- Clock skew may cause synchronous circuit behaves asynchronously

Static hazards

 
If transition is within the same group in the K-map, no hazard



- static 1-hazard



- static 0-hazard

 

Dynamic hazards

- output changes more than once as a result of a single output change
- Elimination of all static hazards eliminates dynamic hazards.