

VE270 Final Exam Review

Register, Shifter, Memroy, PLD


Shi Li

2019.12.10

1. Register

Basic register



- Used to store data.

 

1. Register

Register with load


- Add a synchronous load signal.

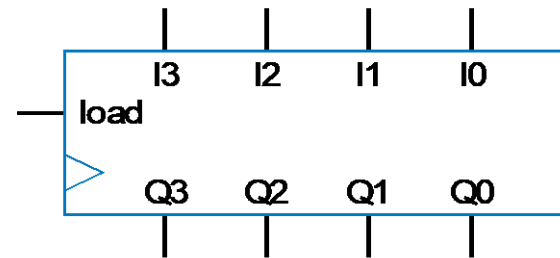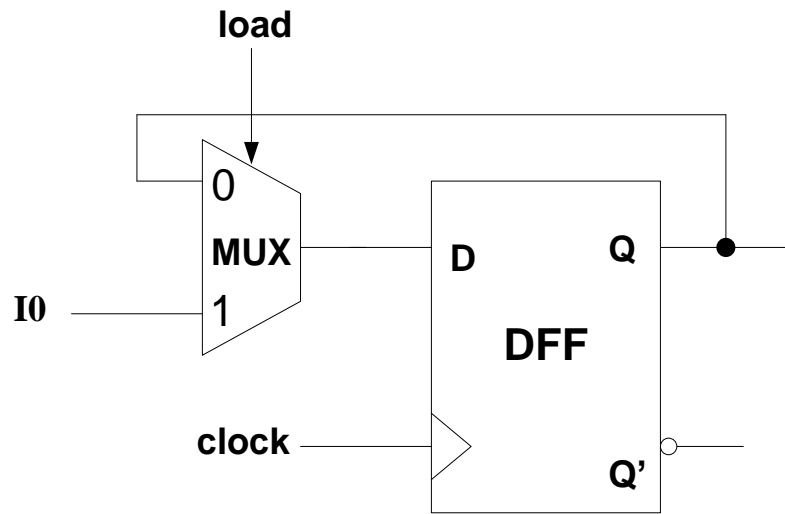

1. Register

Register file


- Used to store a lot of data.

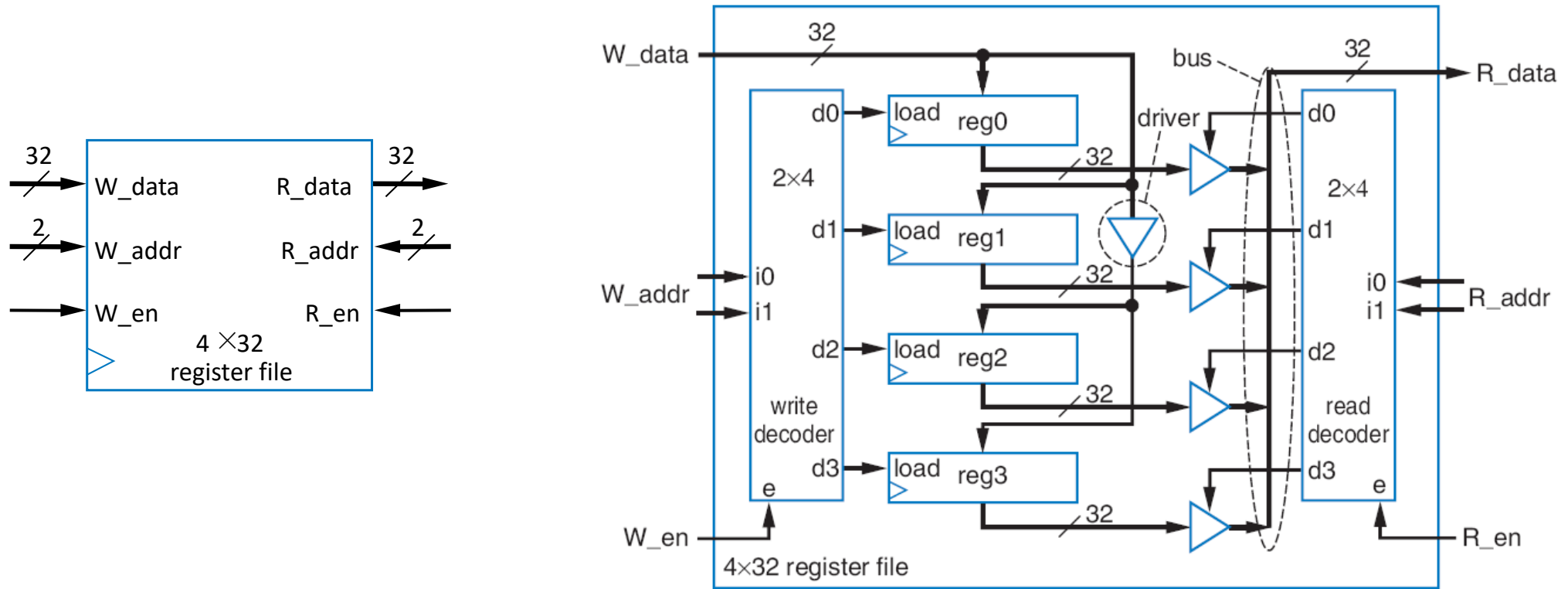


1. Register

Shift register (not shifter) & Rotate register

- Shift or rotate, every clock cycle.

 

	IN	OUT(3:0)
Initial value:	0	0110
rising edge:	0	0011
rising edge:	0	0001
rising edge:	0	0000
rising edge:	1	1000
rising edge:	0	0100

 


	OUT(3:0)
Initial value:	0110
rising edge:	0011
rising edge:	1001
rising edge:	1100
rising edge:	0110
rising edge:	0011

1. Register

Universal shift register

- Shift or rotate, every clock cycle.
- Exercise: Write Verilog code for it.

Inputs		Action
Sh (Shift)	L (Load)	
0	0	no change
0	1	load
1	X	Shift Right

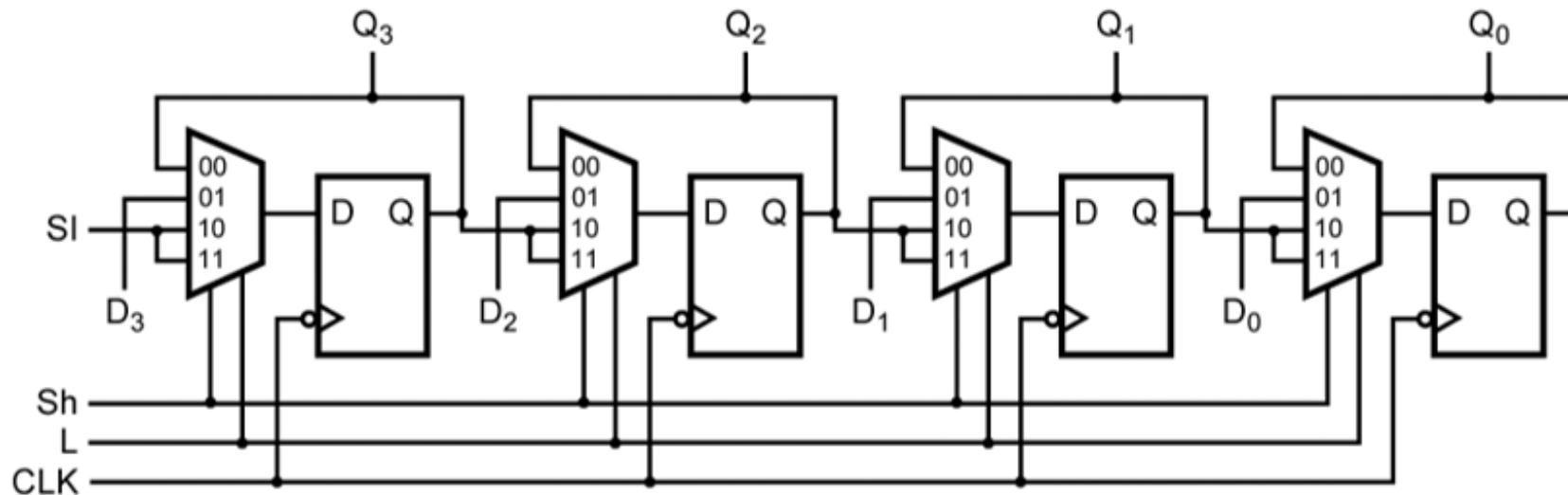

1. Register



Exercise Solution

```
module Universal_Shift_Reg (D, Q, SI, Sh, L, Clk);  
    input  SI, Sh, L, Clk;  
    input  [3:0] D;  
    output [3:0] Q;  
    reg    [3:0] Q;  
  
    always @ (posedge clock)  
    begin  
        if (Sh == 1)  
        begin  
            Q[2:0] <= Q[3:1];  
            Q[3]   <= SI;  
        end  
        else if (L == 1)  
            Q <= D;  
        end  
    endmodule
```

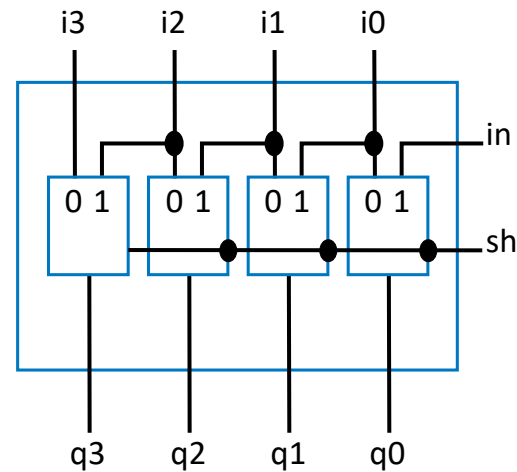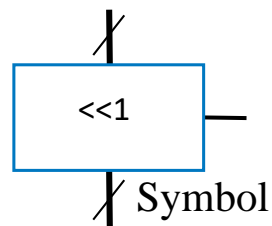
2. Shifter (not shift register)

Basic shifter

- Combinational component, not sequential! (do not depend on Clk)
- Shift left once = multiply by 2
- Shift right once = divide by 2




Shifter with left
shift or no shift

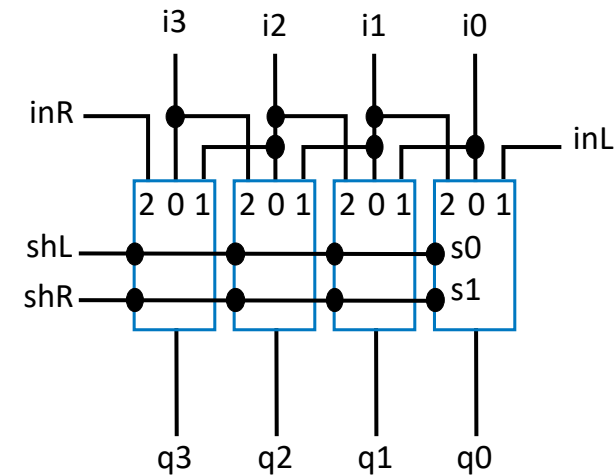

Shifter with left
shift, right shift,
and no shift


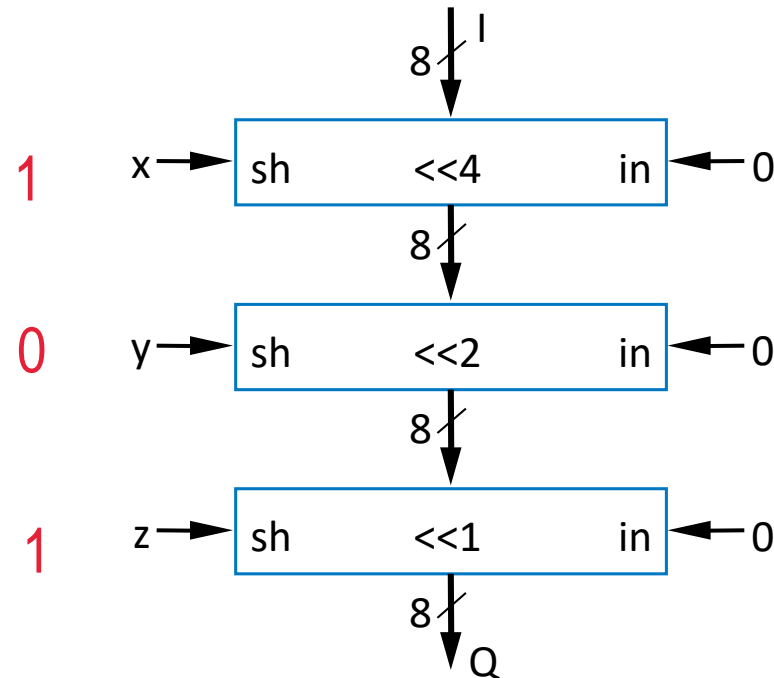
2. Shifter (not shift register) Bigger shifter

- How to use bigger shifter to shift by any amount?
- Suppose the input is 11111111, how to set xyz so that the output will be 11100000?



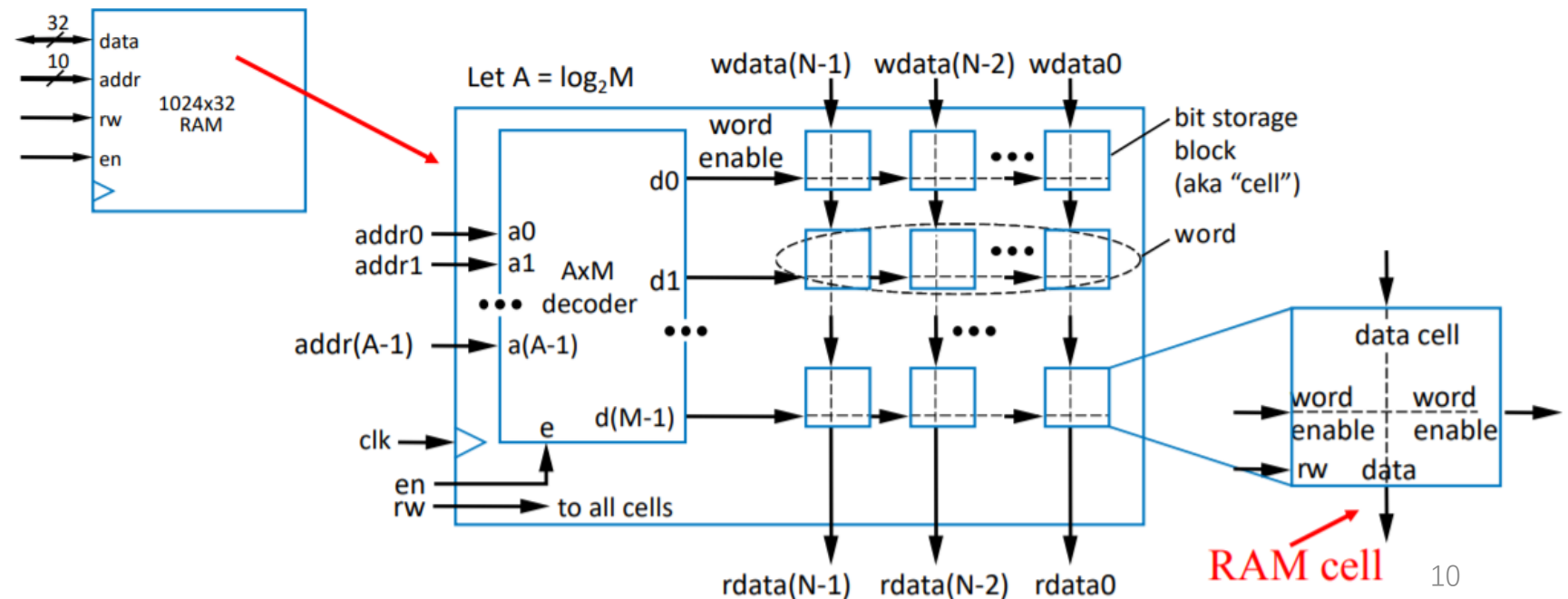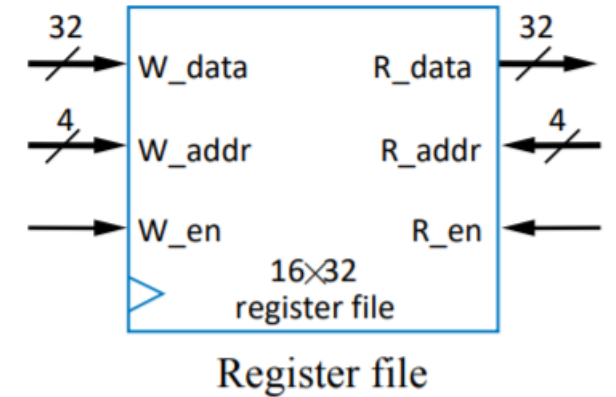3. Memory Concept


- Random Access Memory (RAM)
 - Similarity to register file: read/write by address
 - Difference to register file: RAM is larger, slower, implemented on a separate device



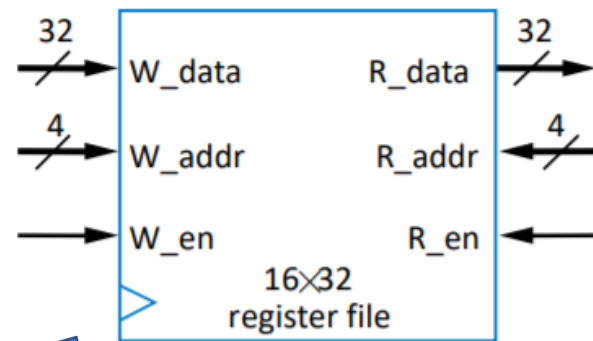
3. Memory

Concept: Random Access Memory (RAM)

- Similarity to register file: read/write by address
- Difference to register file: RAM is larger, slower, implemented on a separate device



Register file

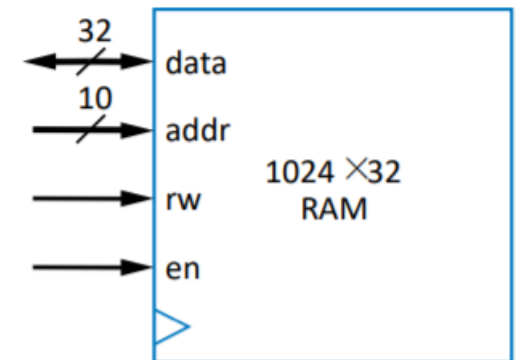


RAM block symbol



3. Memory


Concept: Random Access Memory (RAM)

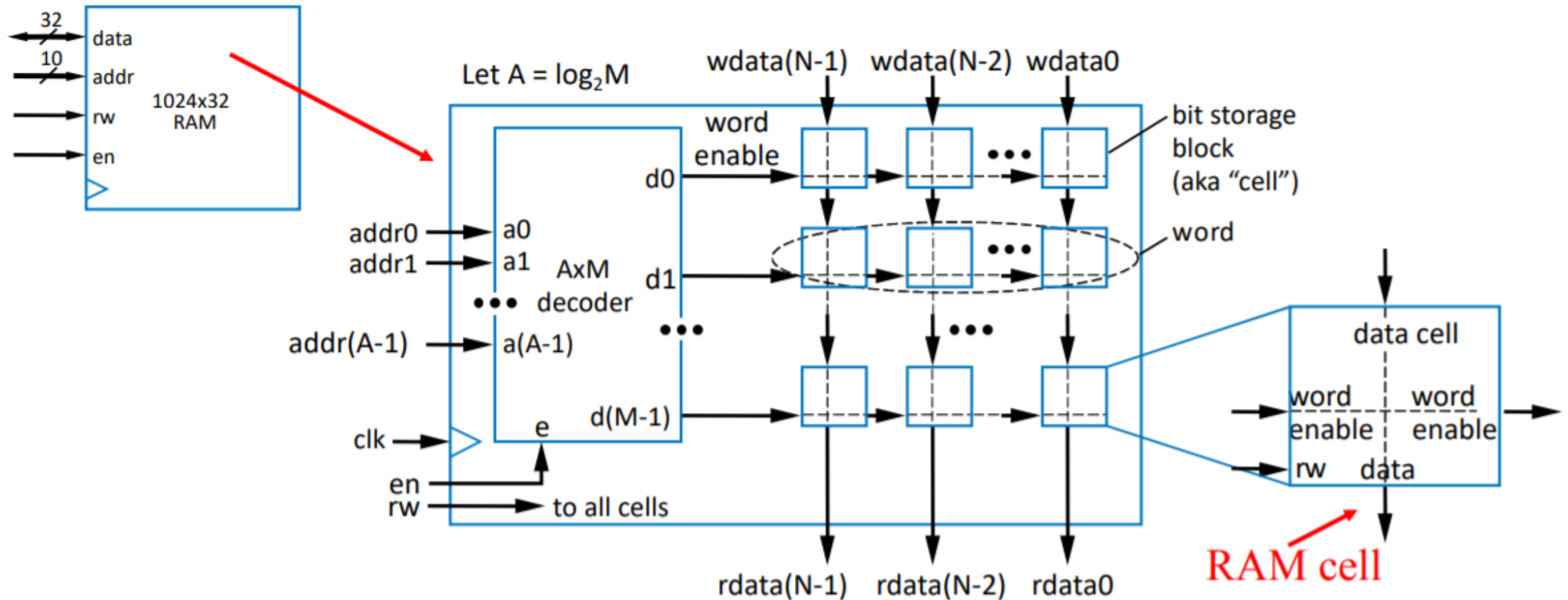



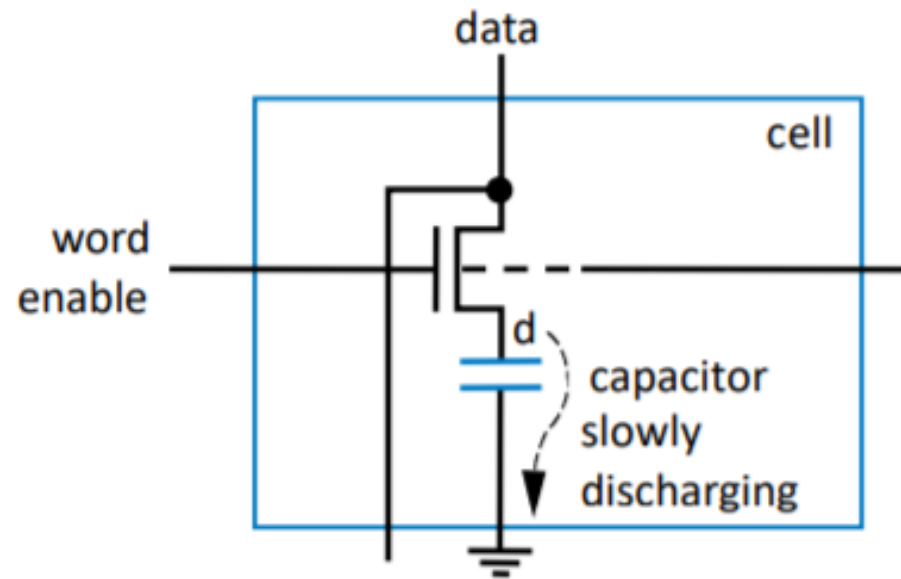
3. Memory

Concept: Dynamic RAM (DRAM)

- 1 transistor and 1 capacitor
- Why use DRAM? Cheaper, larger.





Example: Intel Nehalem 4-core processor

 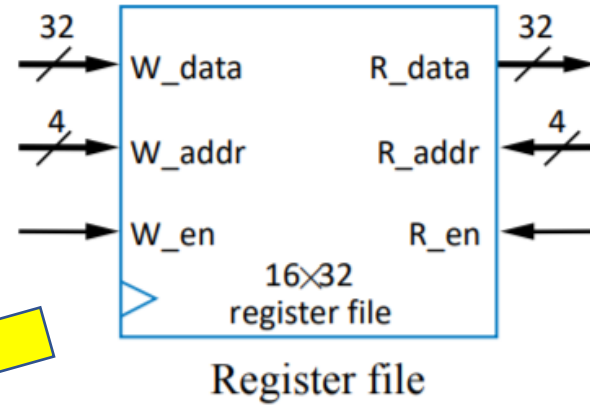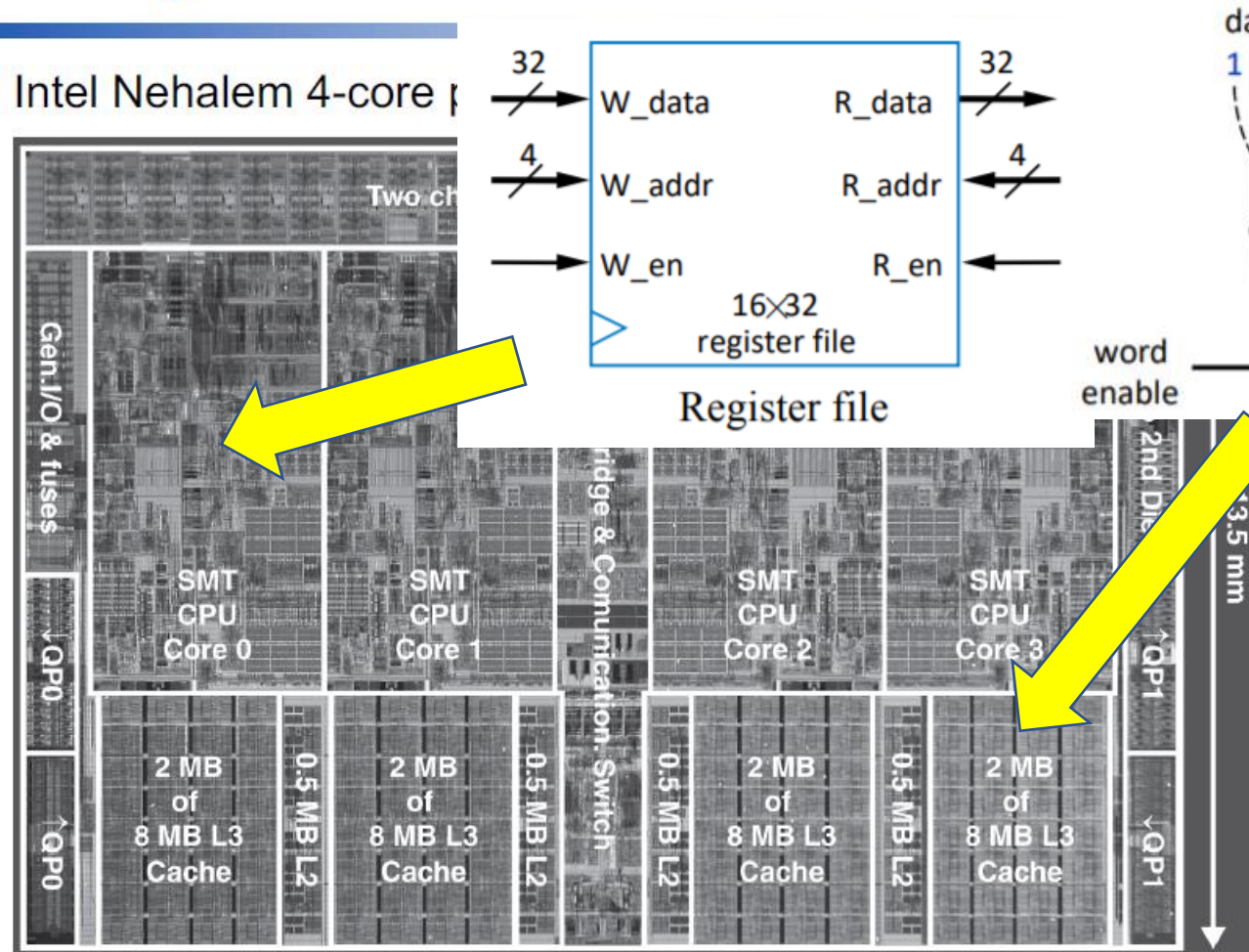

SRAM

DRAM

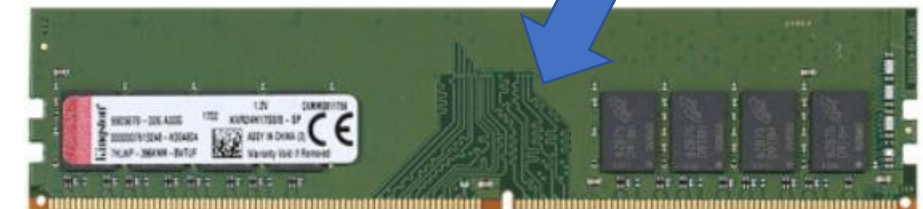 


Per core: 32KB L1 I-cache, 32KB L1 D-cache, 512KB L2 cache

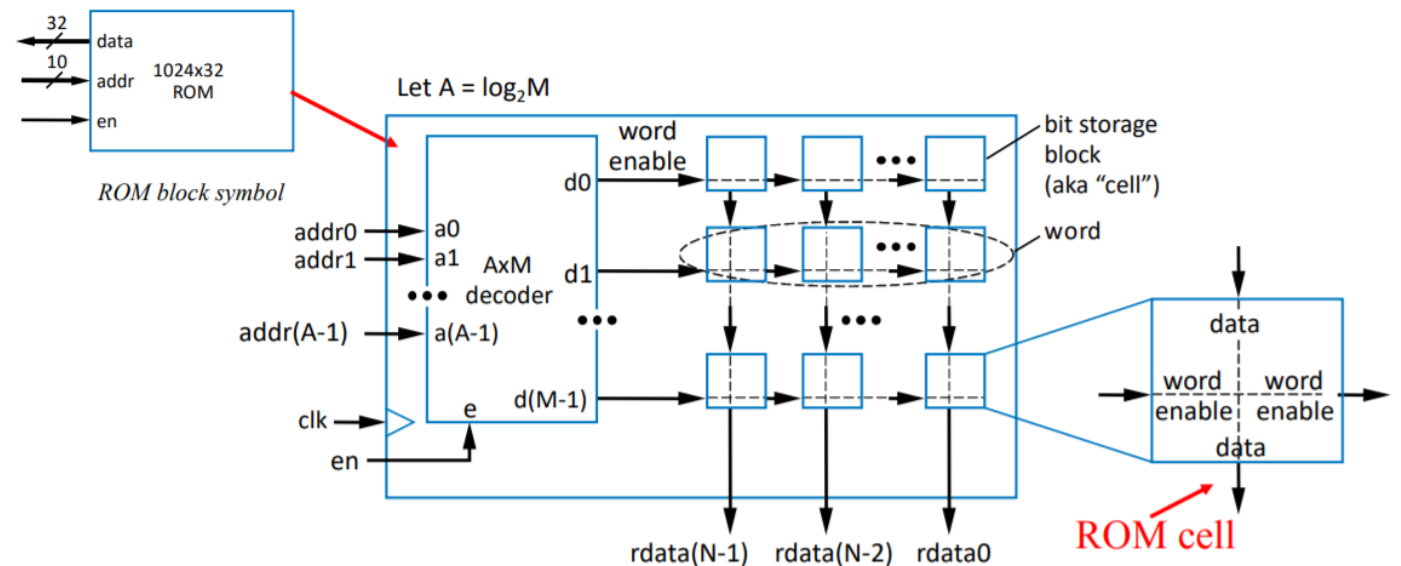3. Memory

Concept: Read-Only Memory (ROM)

- Memory that can only be read, but cannot be written
- So... Why use ROM?
 - Small
 - Non-volatile
 - Fast
 - Low power
- Structure: Similar to RAM
- Type: EPROM, EEPROM...



3. Memory

Concept: Read-Only Memory (ROM)

- Where can you find ROM in your computer?
- Eg. Basic Input & Output System (BIOS) program is stored in ROM on your motherboard.




(The ROM in the picture is actually in one of the computers in JI...)

4. Programmable Logic Devices (PLD) Concept

- Simple Simple programmable logic devices (SPLD)
 - Programmable logic array (PLA)
 - Programmable array logic (PAL)
- Complex programmable logic array (CPLD)
- Field-programmable gate array (FPGA)

4. Programmable Logic Devices (PLD)

Concept: PLA & PAL

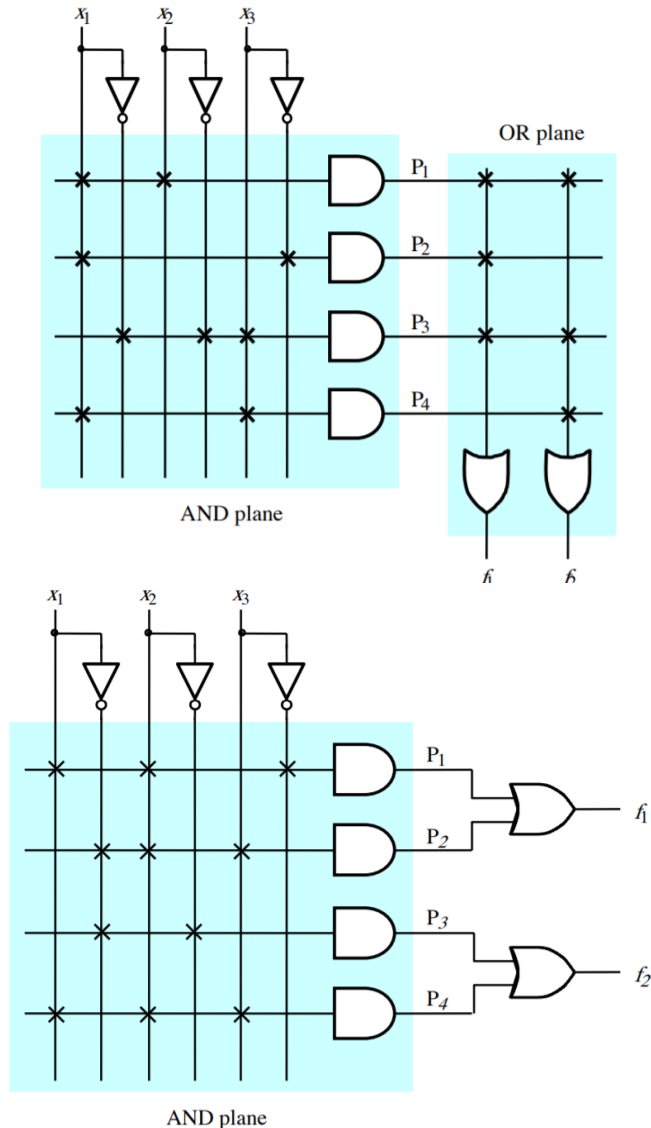

BASIS FOR COMPARISON

PLA

PAL

Stands for

Programmable Logic
Array

Programmable Array Logic

Construction

Programmable array of
AND and OR gates.

Programmable array of AND
gates and fixed array of OR
gates.

Availability

Less prolific

More readily available

Flexibility

Provides more
programming flexibility.

Offers less flexibility, but more
likely used.

Cost

Expensive

Intermediate cost

Number of
functions

Large number of
functions can be
implemented.

Provides the limited number of
functions.

Speed


Slow

High

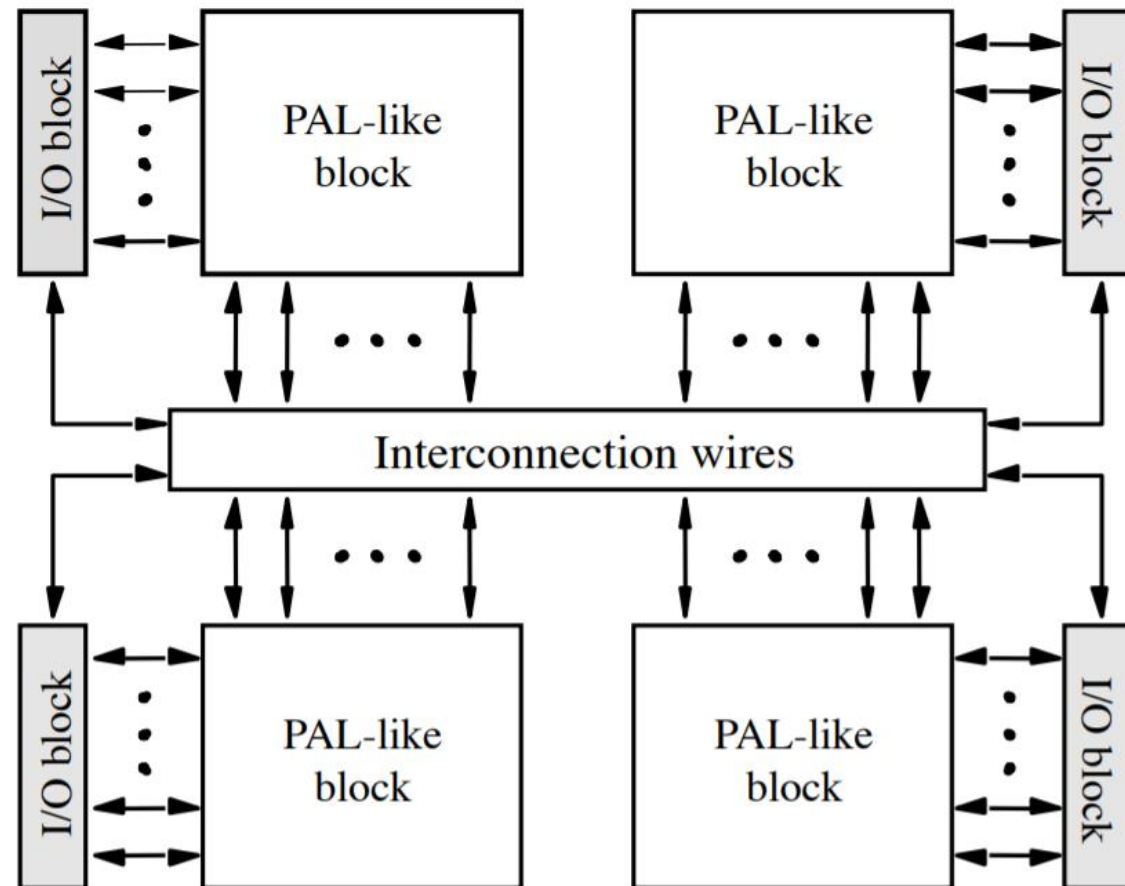4. Programmable Logic Devices (PLD)

Concept: CPLD

- More complex than PLA or PAL
- Provide more I/O




4. Programmable Logic Devices (PLD)


Concept: FPGA

- Reprogrammable
 - SRAM-based (volatile, what we use in lab)
 - EEPROM-based (Flash-based)
- One-time programmable (OTP)
 - Anti-fuse-based FPGA
 - Anti-fuse: apply high-voltage/temperature: insulating->conducting
 - EPROM-based

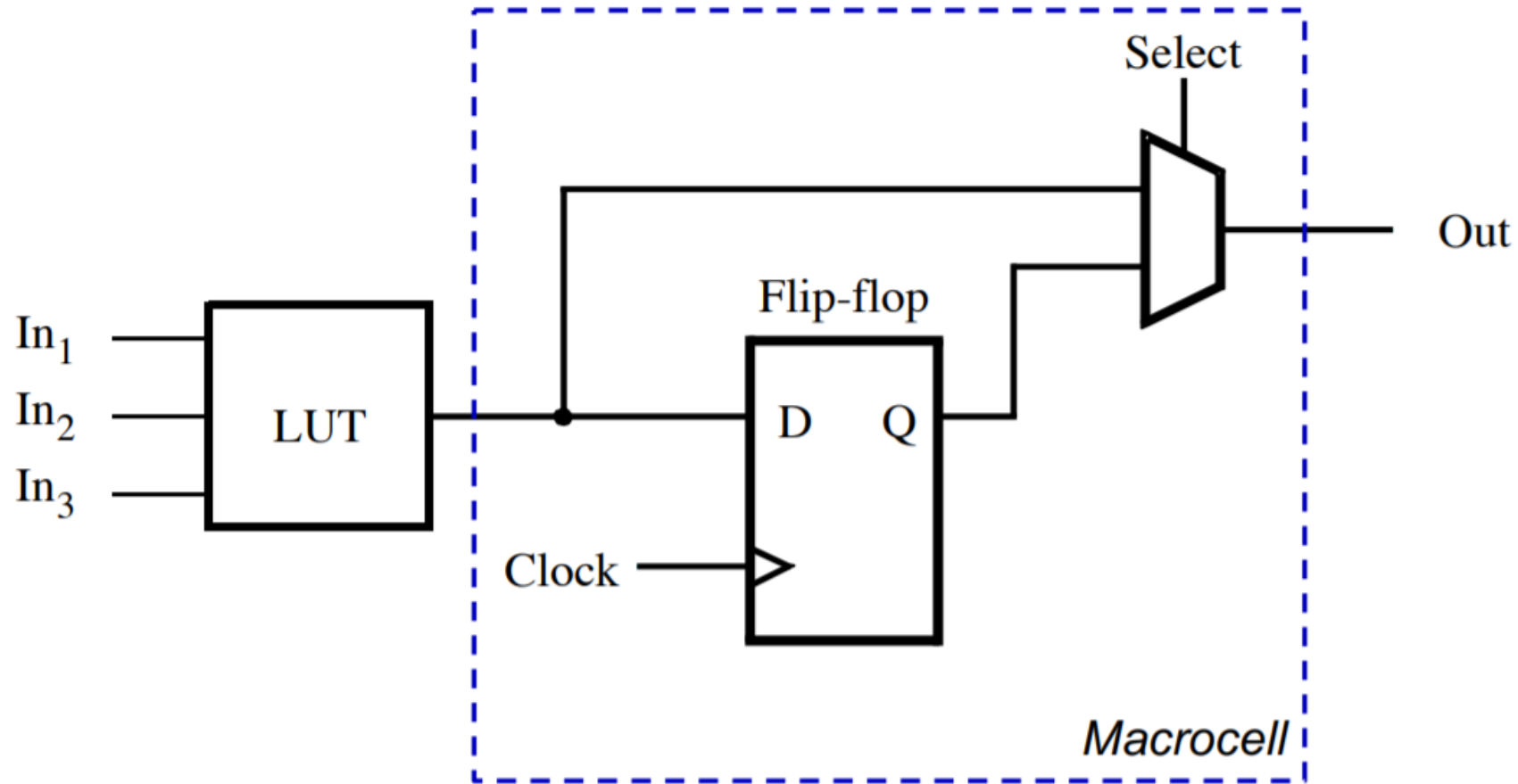4. Programmable Logic Devices (PLD) Configurable Logic Block (CLB) in FPGA



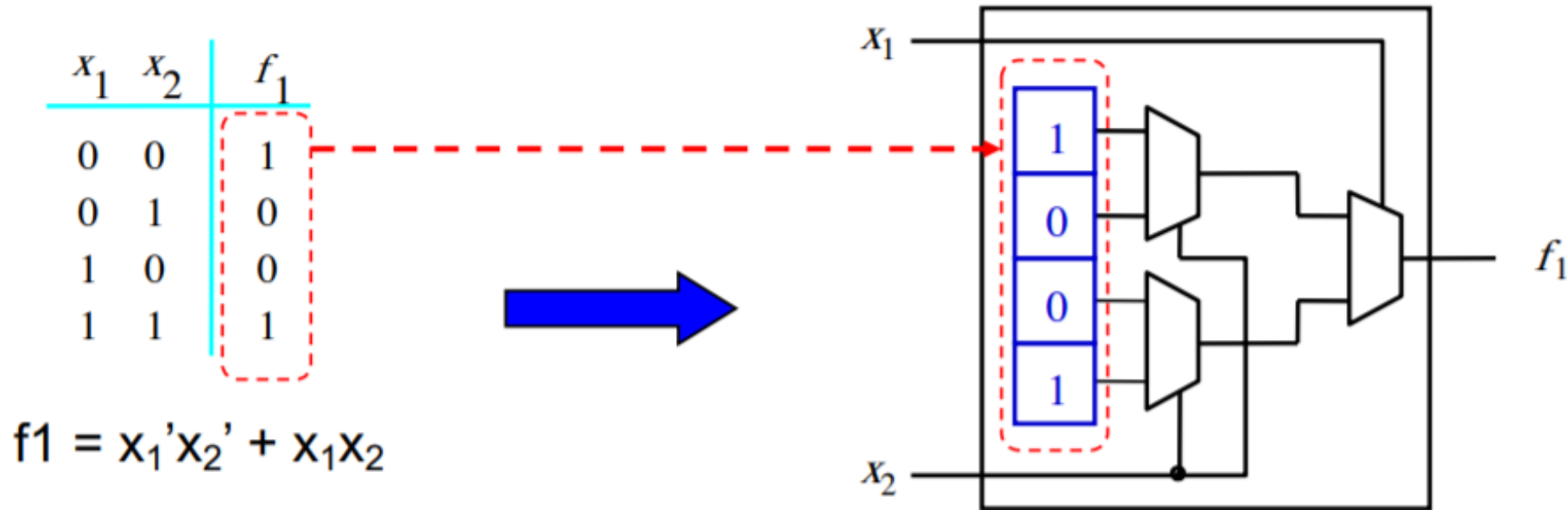4. Programmable Logic Devices (PLD) Look-Up Table (LUT) in FPGA



Thanks for your support!
Good luck and see you VE370 :)