

VE270 RC Week 8

Register & Shifter & FSM


Shi Li

2019.10.9

1. Register

Basic register



- Used to store data.

 

1. Register



Register with load

- Add a synchronous load signal.

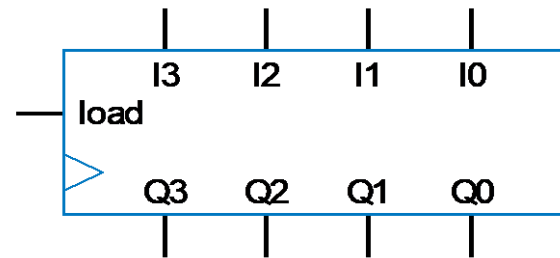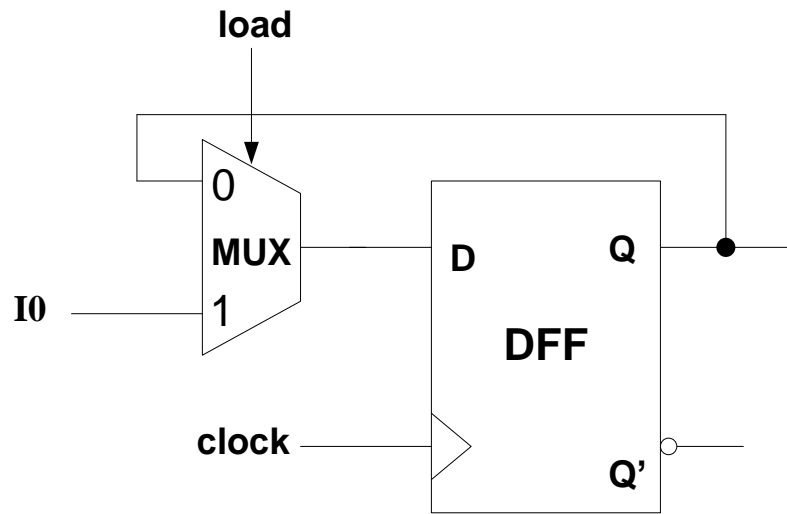

1. Register Register file


- Used to store a lot of data.

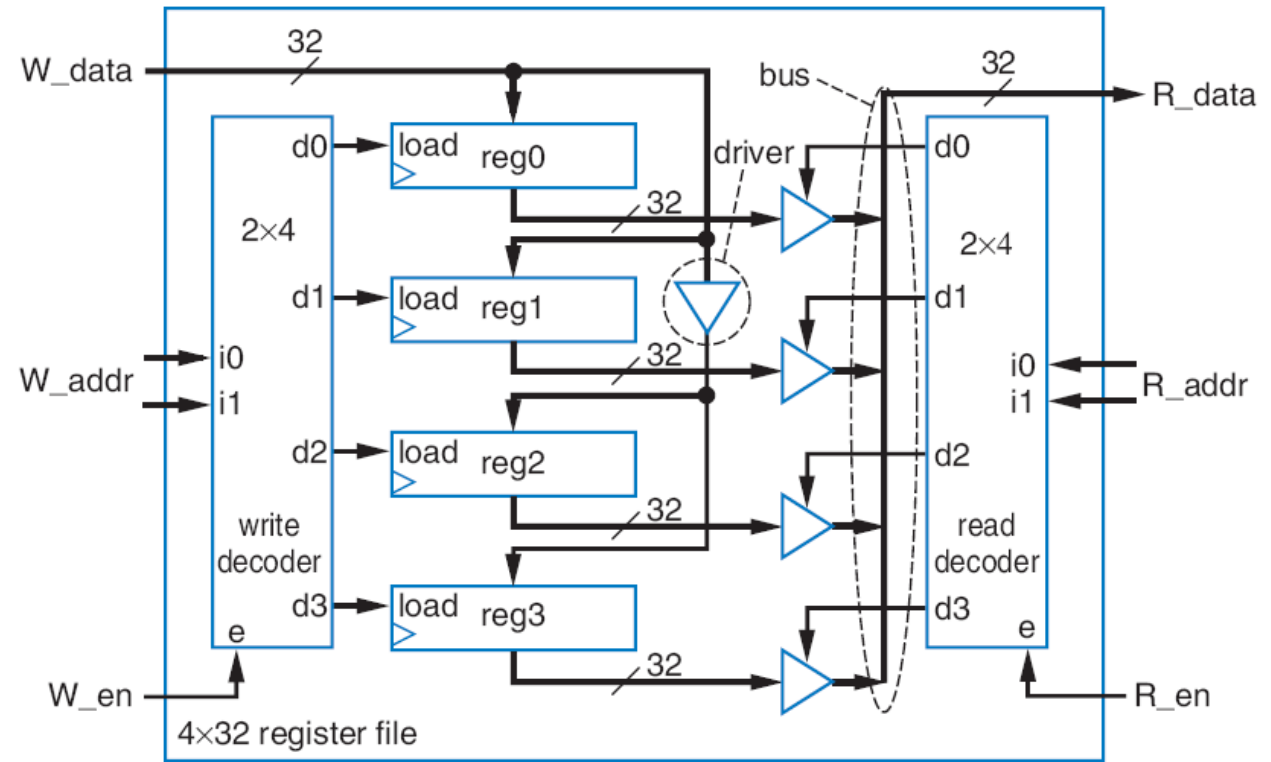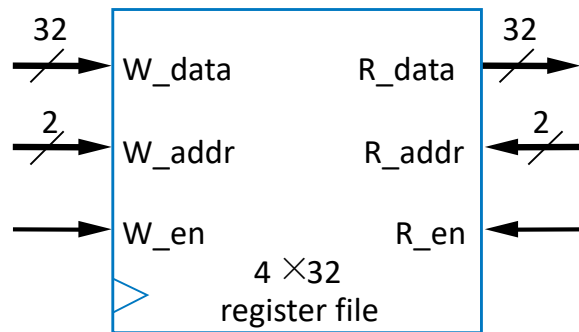


1. Register

Shift register (not shifter) & Rotate register

- Shift or rotate, every clock cycle.

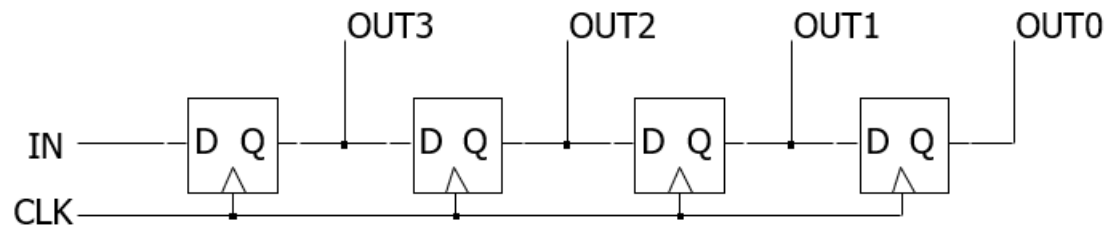

	IN	OUT(3:0)
Initial value:	0	0110
rising edge:	0	0011
rising edge:	0	0001
rising edge:	0	0000
rising edge:	1	1000
rising edge:	0	0100

 


	OUT(3:0)
Initial value:	0110
rising edge:	0011
rising edge:	1001
rising edge:	1100
rising edge:	0110
rising edge:	0011

1. Register

Universal shift register

- Shift or rotate, every clock cycle.
- Exercise: Write Verilog code for it.

Inputs		Action
Sh (Shift)	L (Load)	
0	0	no change
0	1	load
1	X	Shift Right

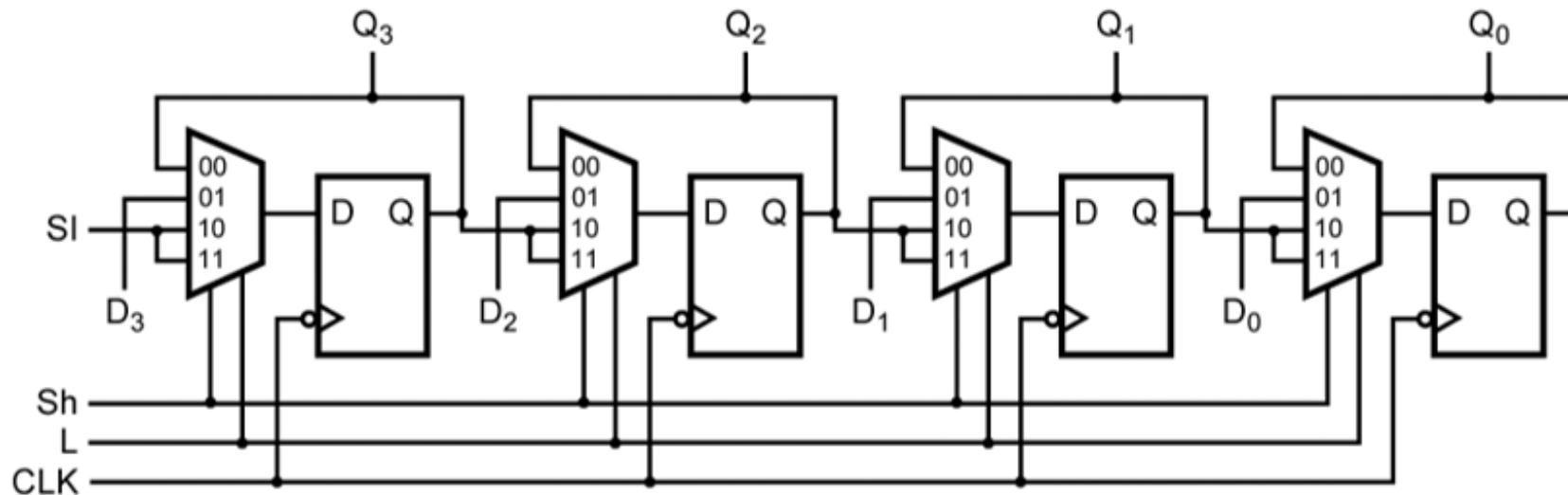

1. Register

Exercise Solution



```
module Universal_Shift_Reg (D, Q, SI, Sh, L, Clk);
    input  SI, Sh, L, Clk;
    input  [3:0] D;
    output [3:0] Q;
    reg    [3:0] Q;

    always @ (posedge clock)
    begin
        if (Sh == 1)
        begin
            Q[2:0] <= Q[3:1];
            Q[3]   <= SI;
        end
        else if (L == 1)
            Q <= D;
        end
    end
endmodule
```

  
2. Shifter (not shift register)

Basic shifter

- Combinational component, not sequential! (do not depend on Clk)
- Shift left once = multiply by 2
- Shift right once = divide by 2



Shifter with left
shift or no shift

 


Shifter with left
shift, right shift,
and no shift

 2. Shifter (not shift register)


Bigger shifter

- How to use bigger shifter to shift by any amount?
- Suppose the input is 11111111, how to set xyz so that the output will be 11000000?




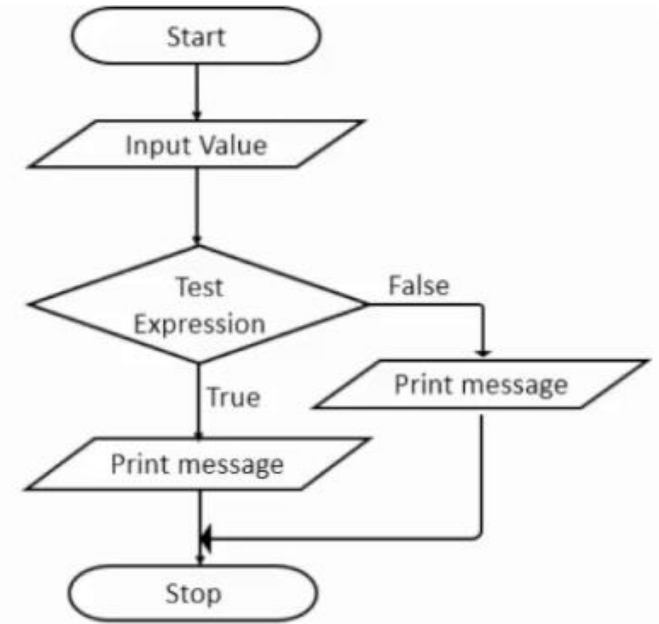3. FSM Concept

- To some extent, similar to program flowchart.
- One of the most essential concepts in VE270.
- It contains:
 - Set of states
 - Set of inputs & outputs
 - Initial state
 - Set of transitions
 - Set of actions
- What are they in this FSM?




Inputs: b; Outputs: x

 

 
3. FSM Concept

- Solution:
 - Set of states ({Off, On1, On2, On3})
 - Set of inputs & outputs (In: {b}, Out: {x})
 - Initial state (Off)
 - Set of transitions (5 transitions here)
 - Set of actions ($x=0$ in Off, $x=1$ in On1, ...)



3. FSM

State diagram & State table

 

3. FSM


Pay attention to State Transition Property!

- Only one condition should be true
- One condition must be true
- All conditions must be considered

3. FSM

 Example: Digital lock (lecture notes review)

- Unlock door ($u=1$) only when buttons pressed in sequence:
 - start, then red, blue, green, red
- Input buttons: s, r, g, b
- Input a indicates that some color button pressed
- FSM
 - Wait for start ($s=1$) in “Wait”
 - Once started, go to “Start”, then
 - If see red, go to “Red1”
 - Then, if see blue, go to “Blue”
 - Then, if see green, go to “Green”
 - Then, if see red, go to “Red2”, and $u=1$
 - Wrong button at any step, return to “Wait”, without opening door




Q: Can you trick this FSM to open the door, without knowing the code?

A: Yes, hold all buttons simultaneously

3. FSM

 Example: Digital lock (lecture notes review)



- **New transition conditions** detect if wrong button pressed, returns to “Wait”

3. FSM

Example: Digital lock (lecture notes review)

- Recall code detector FSM

- Do the transitions obey the two required transition properties?

NO!

- How would it go wrong?

E.g. $arbg = 1111$

How to solve?

Answer: ar should be $arb'g'$
(likewise for ab , ag , ar)

